
ELEC 374

Digital Systems Engineering

Winter 2023

CPU Design Project Tutorial

Ahmad Afsahi

Course web site

<https://onq.queensu.ca/d2l/home/758443>

Instruction Set Architecture

- **Instruction Set Architecture (ISA):** is an abstract interface between the hardware and the lowest level software of a machine that encompasses all necessary information to write a machine language program that will run correctly, including instructions, registers, memory access, I/O, etc.
 - It involves decisions regarding registers, memory addressing, addressing modes, instruction operands, available operations, control flow instructions, and instruction encoding.
- **Evaluating ISA:**
 - **Design-time metrics:**
 - ❖ Can it be implemented? With what performance, and at what costs (design, fabrication, test, packaging), with what power, and with what reliability?
 - ❖ Can it be programmed? Ease of compilation?
 - **Static Metrics:**
 - ❖ How many bytes does the program occupy in memory?
 - **Dynamic Metrics:**
 - ❖ How many instructions are executed? How many bytes does the processor fetch to execute the program?
 - ❖ How many clocks are required per instruction?
 - ❖ How “lean” a clock is practical?

RISC Design Principles

1. Simplicity favours regularity

- Fixed size instructions
- Instructions to have (mostly) the same number of operands
- Opcode always a few bits of an instruction

2. Smaller is faster

- Limited instruction set
- Limited number of registers in register file
- Limited number of addressing modes

3. Good design demands good compromises

- Fixed size instructions → requiring different (but small number of) kinds of instruction formats

4. Make the common case fast

- Arithmetic operands from the register file (Load-Store machine)
- Allow instructions to contain immediate operands


Designing a Simple RISC Computer (Mini SRC)

◦ Mini SRC is a variant of SRC in Lab Reader

◦ Processor State:

PC<31..0>:	32-bit Program Counter (PC)
IR<31..0>:	32-bit Instruction Register (IR)
R[0..15]<31..0>:	Sixteen 32-bit registers named R[0] through R[15]
R[0..7]<31..0>:	Eight general-purpose registers
R[8..11]<31..0>:	Four Argument Registers
R[12..13]<31..0>:	Two Return Value Registers
R[14]<31..0>:	Stack Pointer (SP)
R[15]<31..0>:	Return Address Register (RA)
HI<31..0>:	32-bit HI Register to keep the high-order word of a Multiplication product, or the Remainder of a Division operation
LO<31..0>:	32-bit LO Register to keep the low-order word of a Multiplication product, or the Quotient of a Division operation

Registers

 

Designing a Simple RISC Computer (Mini SRC) - Cont'd

◦ Memory State:

Mem[0..511]<31..0>: 512 words (32 bits per word) of memory

MDR<31..0>: 32-bit memory data register

MAR<31..0>: 32-bit memory address register

◦ I/O State:

In.Port<31..0>: 32-bit input port

Out.Port<31..0>: 32-bit output port

Run.Out: Run/halt indicator

Stop.In: Stop signal

Reset.In: Reset signal

Mini SRC ISA Overview

◦ Instruction Categories:

- Arithmetic and Logical
- Load and Store
- Jump and Branch
- Input and Output
- Special and Miscellaneous

◦ Addressing Modes:

- Direct/Absolute
- Register
- Register indirect
- Indexed
- Immediate
- Relative

◦ Instruction Formats:

Name		Fields				Comments
Field size	31..27 5 bits	26..23 4 bits	22..19 4 bits	18..15 4 bits	14..0 15 bits	All instructions are 32-bit long
R-Format	OP	Ra	Rb	Rc	Unused	Arithmetic/Logical
I-Format	OP	Ra	Rb	Constant C / Unused		Arithmetic/Logical; Load/Store; Imm.
B-Format	OP	Ra	C2	Constant C		Branch
J-Format	OP	Ra	Unused			Jump; Input/Output; Special
M-Format	OP	Unused				Misc.

SRC: Simple RISC Computer

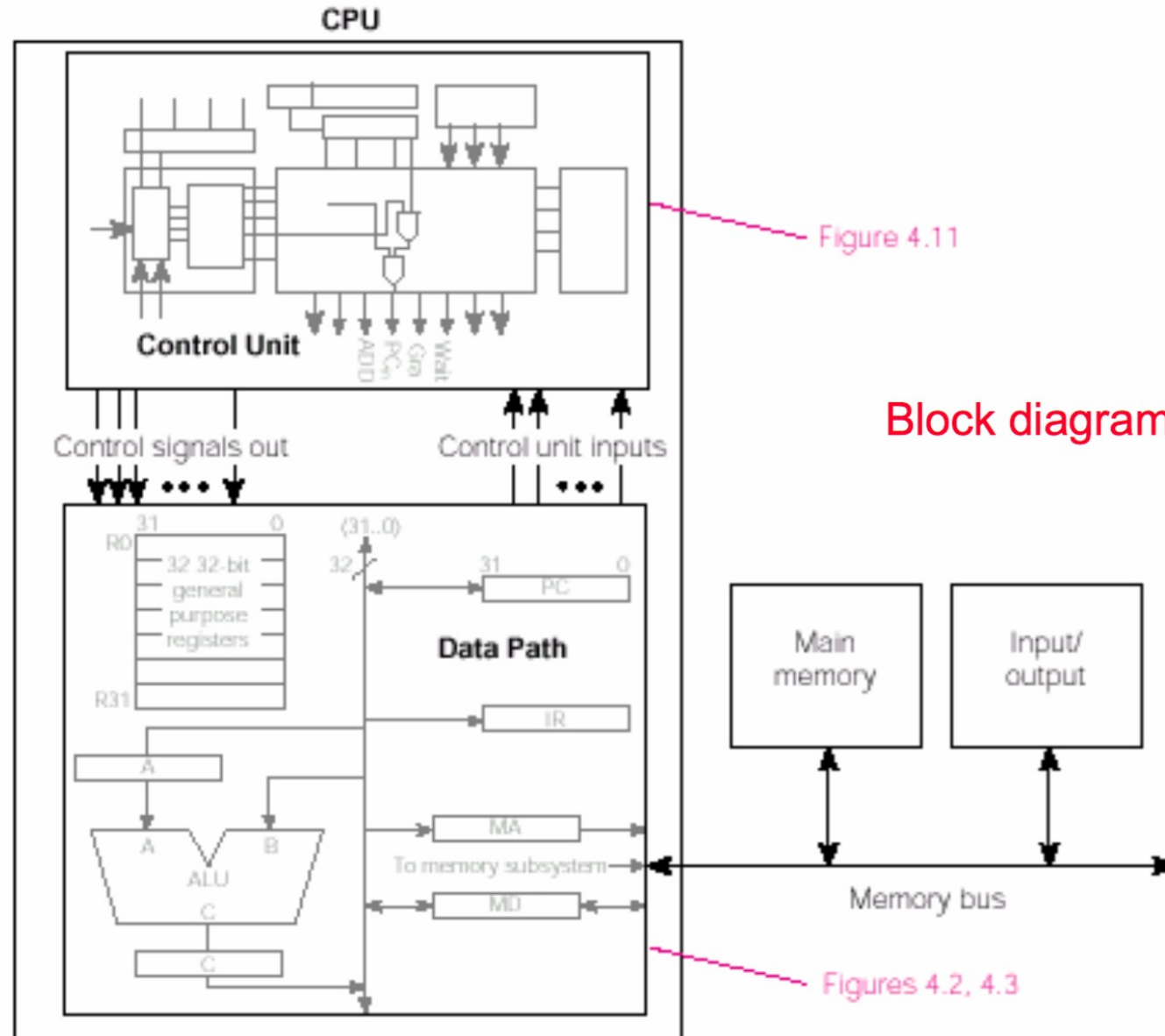



Figure 4.11

Block diagram of SRC

Figures 4.2, 4.3

Reference: Heuring/Jordan, Ch. 4
([Lab Reader](#) in onQ)

SRC: Simple RISC Computer (Cont'd)

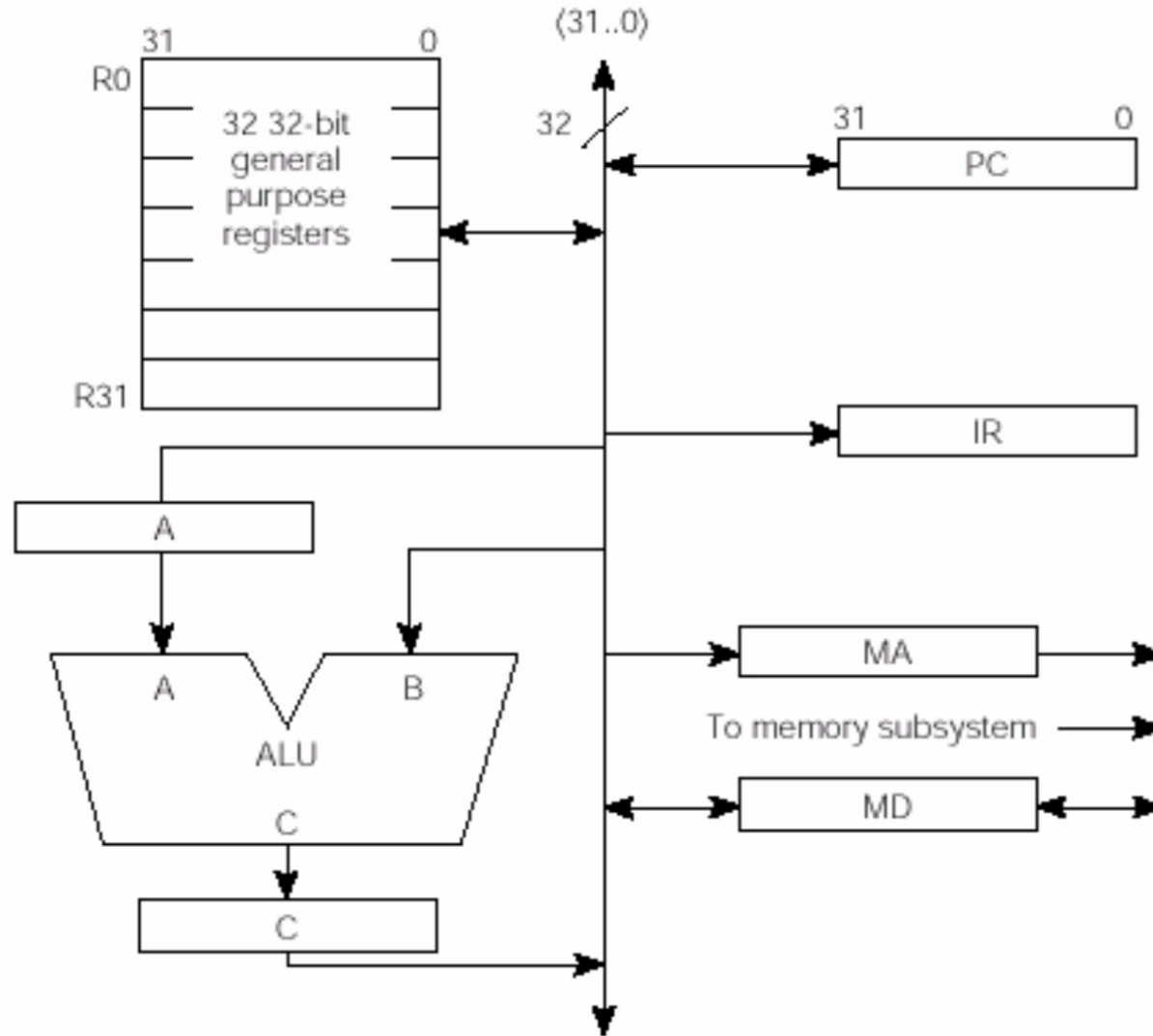


Reference: Heuring/Jordan, Ch. 4
([Lab Reader](#) in onQ)

High-level view of the 1-Bus SRC design

Mini SRC Datapath Design

◦ Lab Phase 1 and Phase 2

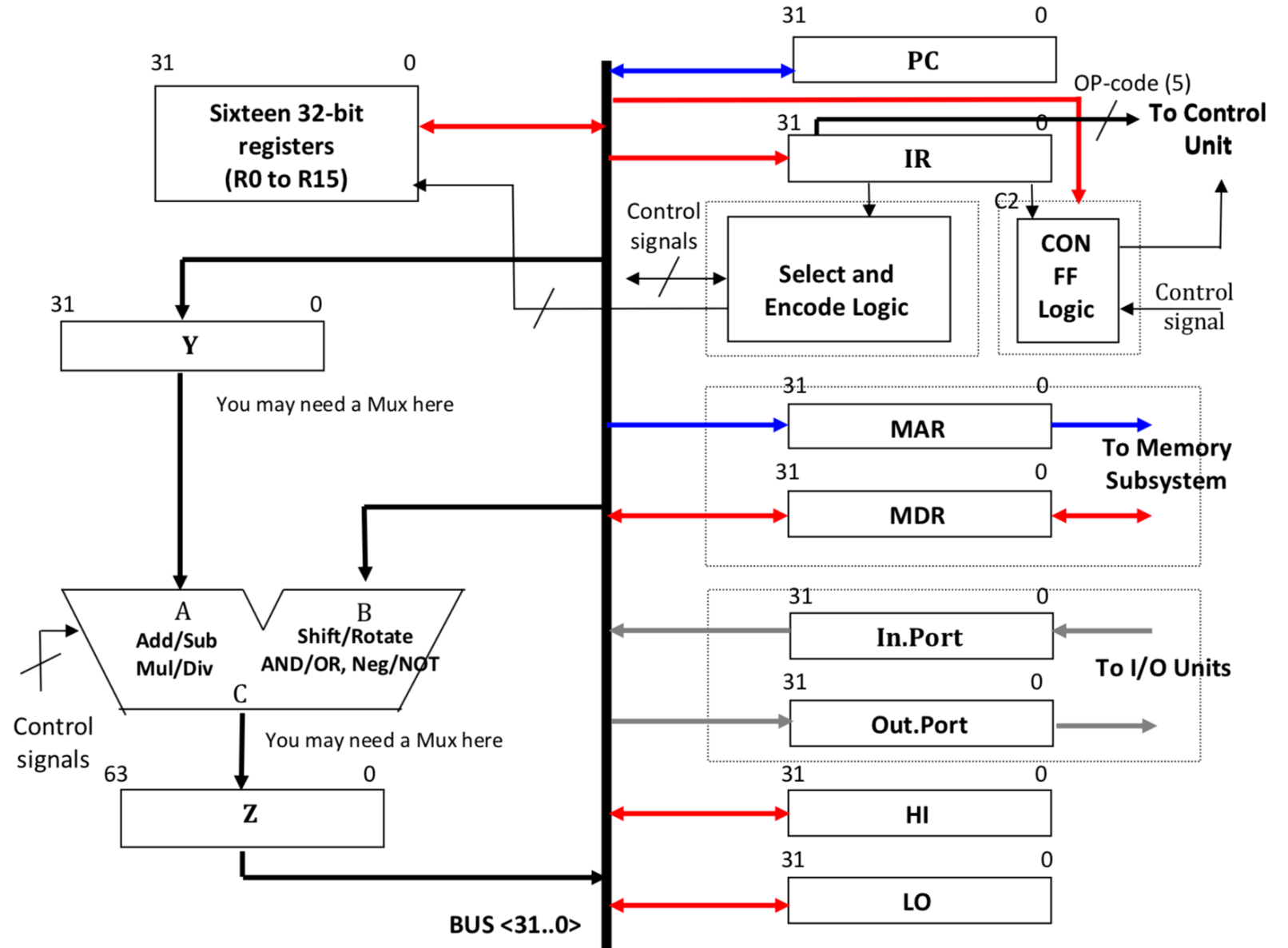You may design your Mini SRC entirely in VHDL or Verilog, or by using a mixed HDL/schematic approach



Mini SRC Datapath Design (Cont'd)

◦ Design Steps in Phase 1:

- Design the registers R0 to R15, PC, IR, Y, Z, MAR, HI, and LO
- Design the bidirectional Bus, and connect the registers that you designed in Step 1 to the Bus
- Design the MDR register and connect it to the BUS. Leave the rest of the Memory Subsystem (connection to the memory module) for Phase 2
- Design your ALU
 - ❖ Start with simple ALU operations such as AND, OR, and NOT. Then,
 - ❖ Design the more involved operations such as ADD/SUB, MUL, and DIV circuitry. Finally, design the rest of the ALU operations.
 - ❖ For the multiplication unit, you are to design your own [32x32 Booth algorithm with bit-pair recoding of multiplier](#).
- Functionally simulate your datapath in Phase 1 and demo it to TA
- Submit your Phase 1 report (one per group)
- Note: Get the required design operations done first. Throughout the term, you are welcome to design and simulate any other advanced design techniques that you learned in class for a bonus mark


Mini SRC Datapath Design (Cont'd)

◦ Control sequence for add R1, R2, R3 instruction:

Control Sequence

Step	Control Sequence
T0	PCout, MARin, IncPC, Zin
T1	Zlowout, PCin, Read, Mdatain[31..0], MDRin
T2	MDRout, IRin
T3	R2out, Yin
T4	R3out, ADD, Zin
T5	Zlowout, R1in

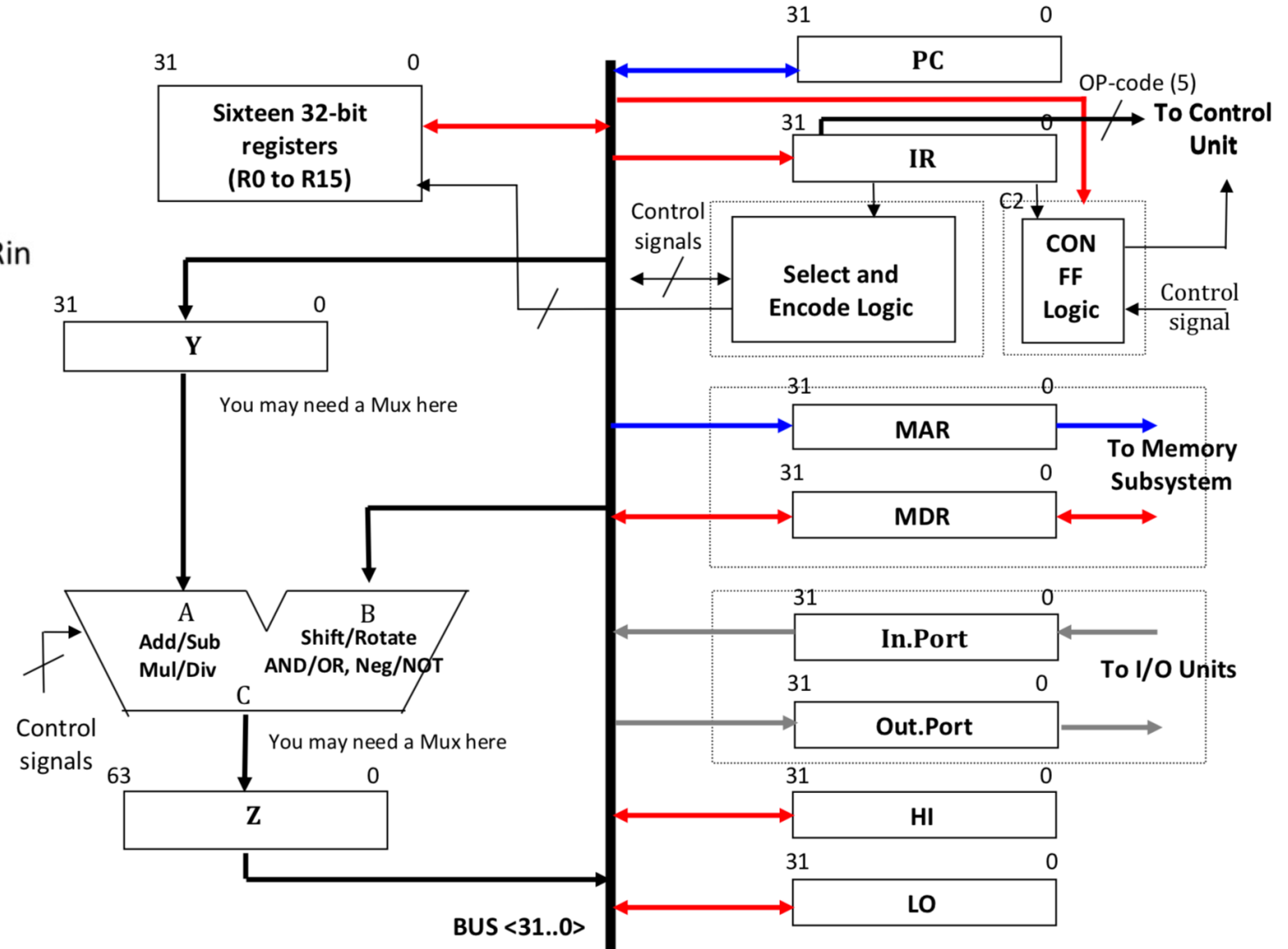Control signals are mostly generated in Phase 3; some in Phase 2.



Mini SRC Datapath Design (Cont'd)

◦ Design Steps in Phase 2:


- Design the remaining parts of the Mini SRC datapath including
 - ❖ “Select and Encode” logic,
 - ❖ “CON FF” logic,
 - ❖ “Memory Subsystem”
 - ❖ “Input/Output” ports
- Functionally simulate your datapath in Phase 1, and demo it to TA
- Submit your Phase 2 report (one per group)
- Note: Get the required design operations done first
 - ❖ You may then go after other advanced design techniques (bonus marks)

Mini SRC Datapath Design (Cont'd)


- Control sequence for Load Indexed (e.g., `ld R2, 10(R1)`) instruction:

Control Sequence: `ld`

Step	Control Sequence
T0	PCout, MARin, IncPC, Zin
T1	Zlowout, PCin, Read, Mdatain[31..0]
T2	MDRout, IRin
T3	Grb, BAout, Yin
T4	Cout, ADD, Zin
T5	Zlowout, MARin
T6	Read, Mdatain[31..0], MDRin
T7	MDRout, Gra, Rin

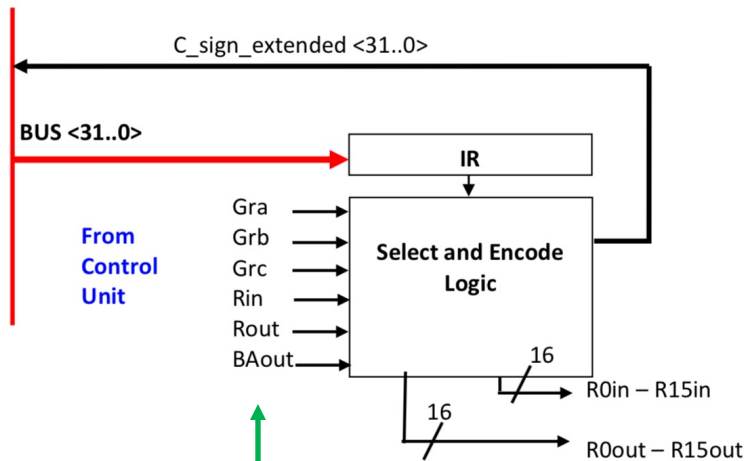


Generated in Phase 3

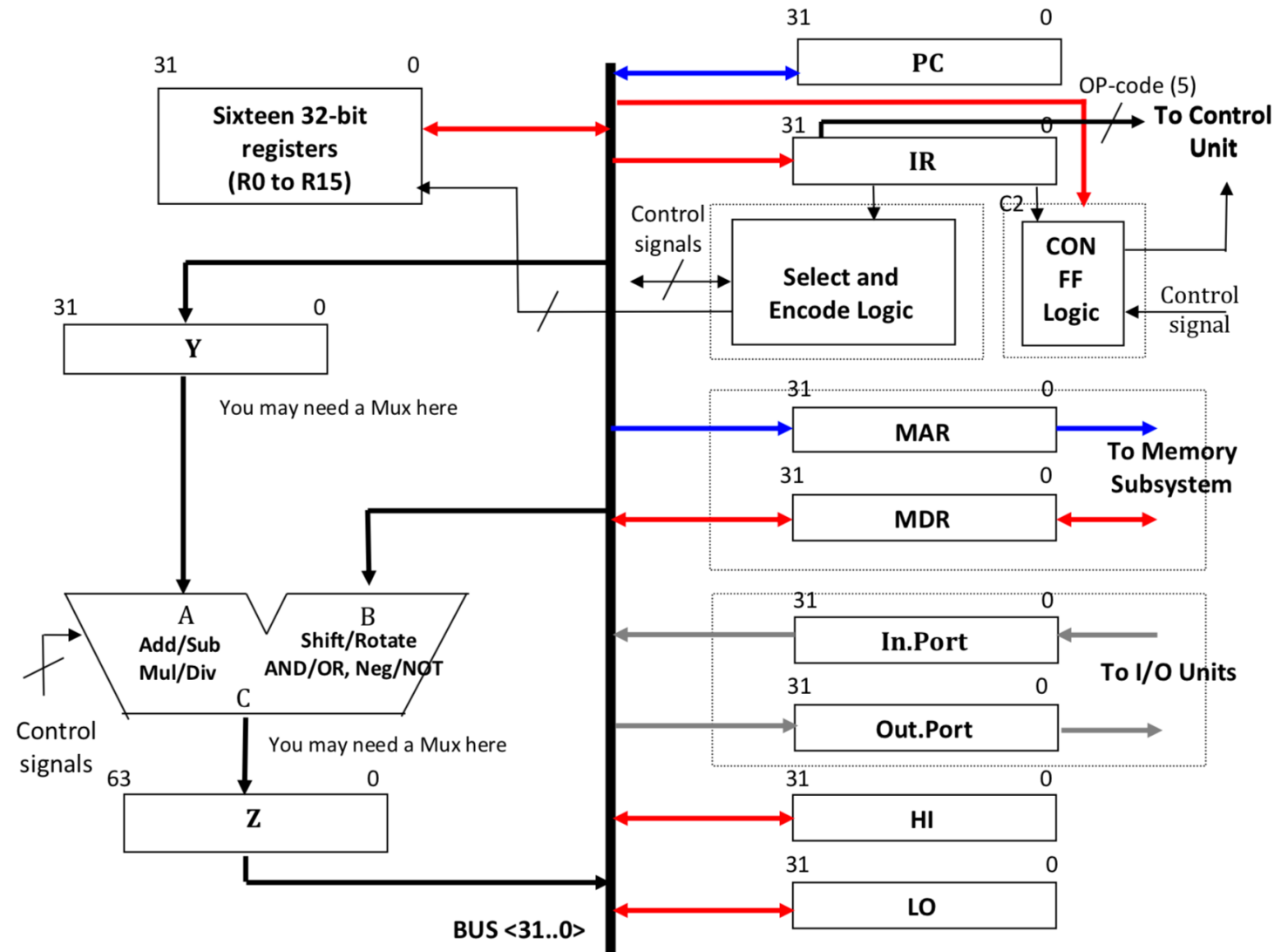

Mini SRC Datapath Design (Cont'd)

° Design Steps in Phase 3:

 - Design the Control Unit of Mini SRC in VHDL or Verilog
- Functionally simulate your Control unit using a given test program and demo it to TA
- Submit your Phase 3 report (one per group)
- Continue your other designs for bonus mark




Mini SRC Datapath Design (Cont'd)


° Design Steps in Phase 4:

- Read the FPGA tutorial and familiarize yourself with the DE0 or DE0-CV development board, its I/O pins, display units, clock circuitry, etc.
- Functionally simulate your Mini SRC processor that you have designed in Phases 1 through 4 using a given test program, and demo it to TA
- Implement and verify the operation of Mini SRC that you have designed and simulated on the development board, and demo it to TA

° Lab Final Report: Submit a detailed final report of your CPU Design Project.

 

DE0

 


DE0-CV

A Potential 2-bus Mini SRC

° The 2-bus SRC design:

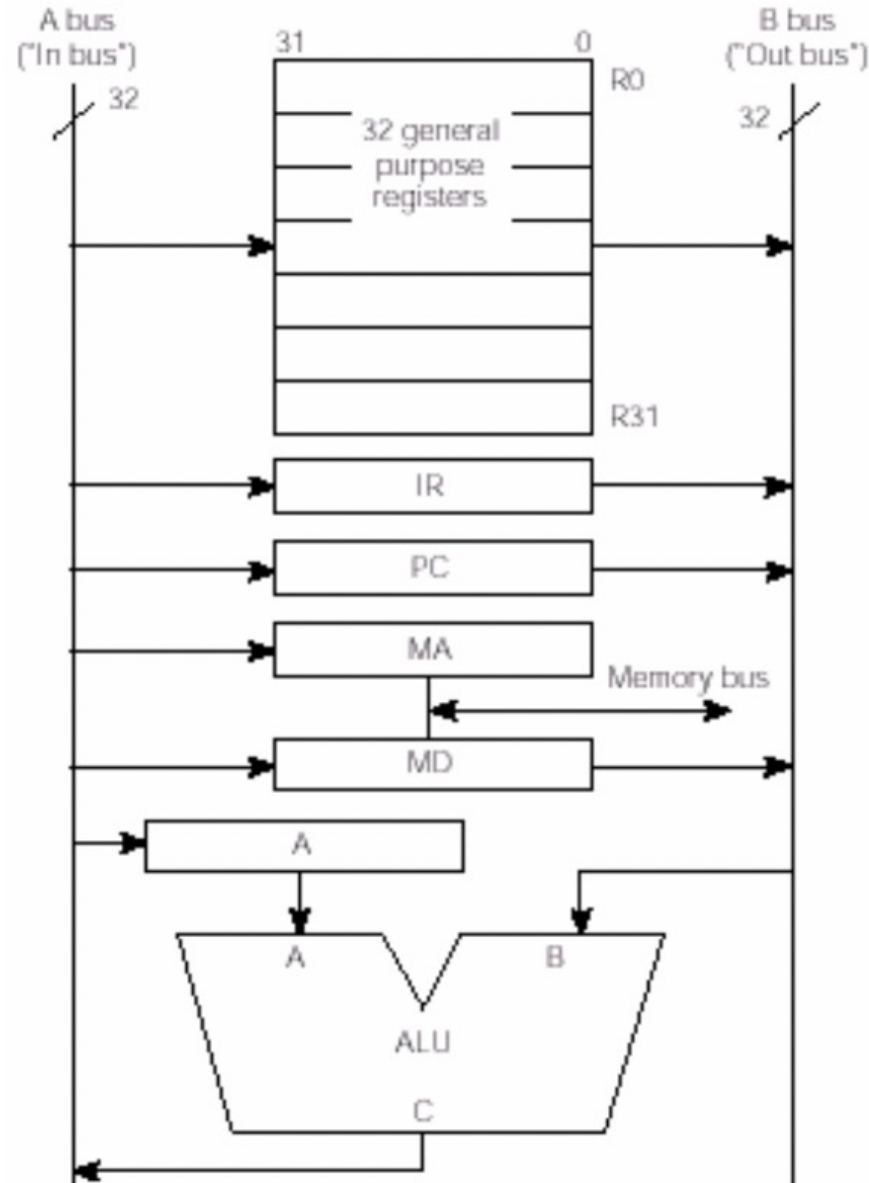- **Bus A carries data going into registers**
- **Bus B carries data being gated out of registers**
- **ALU function $C = B$ is used for all simple register transfers**




Reference: Heuring/Jordan, Ch. 4
([Lab Reader](#) in onQ)

A Potential 3-bus Mini SRC

◦ The 3-bus SRC design:

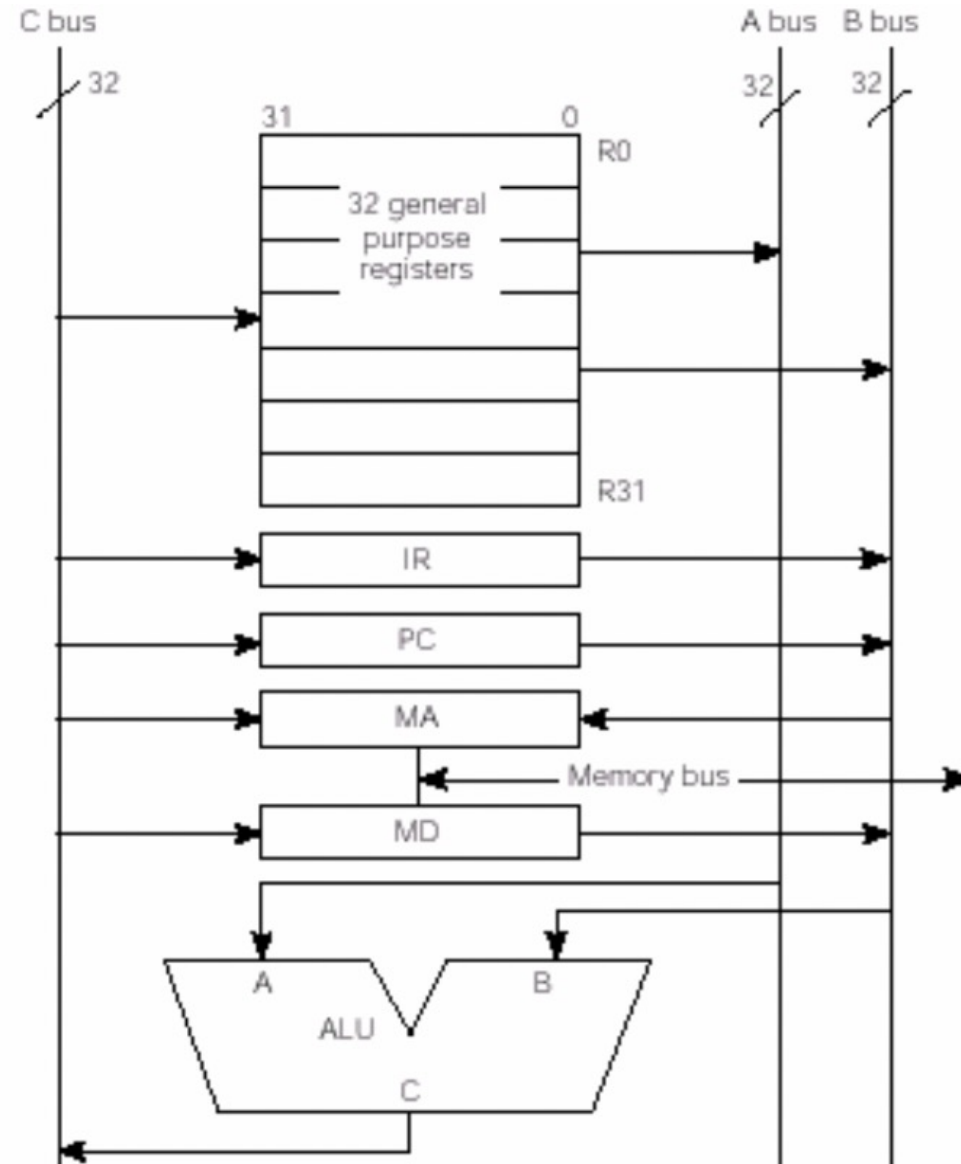- **A-bus is ALU operand 1, B-bus is ALU operand 2, and C-bus is ALU output**
- **Note MA input connected to the B-bus**



Reference: Heuring/Jordan, Ch. 4
([Lab Reader](#) in onQ)

General Guidelines

- Identify your Lab Partner in advance (groups cannot be changed later)
- For each phase, collaborate with your Lab Partner
 - Divide up the required job for each phase between the group members
 - While someone is working on the project with the machine in the Lab, the other group member should work on their own laptop and coordinate things
- Read the descriptions of Lab Phases carefully
- Consult the Lab Reader
- Refer to the Tutorial document on Intel Quartus II and ModelSim
- Consult the Lecture Slides on Computer Arithmetic, VHDL, and Verilog
- Refer to DE0 and DE0-CV User Manuals
- Read the additional reference material on VHDL, Verilog, etc., in the tutorial and on the course website
- Contact TAs and Instructor during/outside Lab hours