

374 Phase 3 Report

March 31, 2023

Group 4:

Liam Salass (20229595)

Abdellah Ghassel (20230384)

"We do hereby verify that this written lab report is our own work and contains our own original ideas, concepts, and designs. No portion of this report has been copied in whole or in part from another source, with the possible exception of properly referenced material"

Table of Contents

Table of Figures	2
Introduction & Motivation	3
The Control Unit	4
The Datapath	18
Xor Module (Bonus)	24
Updated Ram	25
Testbench	26

Table of Figures

Figure 1: Entire waveform of all instructions	28
Figure 2: Instructions 1 to 5	29
Figure 3: Instructions 6 to 11	29
Figure 4: Instructions 13 -18 (note 12 is skipped due to branch)	30
Figure 5: Instrctions 19 to 23	30
Figure 6: Instruction 24 to 28	31
Figure 7: Instruction 29 to 34	31
Figure 8: Instruction 35 to 40	32
Figure 9: Instruction 300 to 304 then baack to 40 - 42 (halt)	32
Figure 10: Contents of Memory after the program ran	32

Introduction & Motivation

In this phase, we focus on the testing of the Control Unit in the Mini SRC, which is a critical component for managing the overall operation of the processor. By designing the Control Unit in Verilog, we aim to consolidate the work accomplished in the previous phases and bring the Mini SRC to a fully functional state.

The motivation behind Phase 3 of the CPU Design Project is to gain a thorough understanding of the Control Unit's role in orchestrating the Mini SRC's operation. By analyzing the interaction between the Control Unit and the datapath components, we aim to ensure the seamless execution of instructions and to further enhance the overall performance of the Mini SRC. Furthermore, this phase provides an opportunity to delve into the intricacies of control signal generation, branching and instruction flow management, and external inputs handling.

The Control Unit

A 32 bit control unit is a component of a CPU that controls the execution of instructions. It functions as a finite state machine, which means that it has a set of states and transitions between them based on some inputs and outputs. The inputs to the control unit are the instruction register (IR) opcode data, which specify the type and format of the instruction to be executed, and the clock signal, which synchronizes the operation of the control unit with other components. The outputs are the control signals that are sent to the arithmetic logic unit (ALU), the registers (Ra, Rb, Rc, Rin, Rout), and other components to perform the required operations.

Depending on the instruction, different states are sequentially cycled through by the control unit. For example, a typical instruction cycle may consist of 3 states: fetch, decode, and execute. In each state, different control signals are sent out to perform specific tasks. For instance, in the fetch state, the control unit sends a signal to the memory to read the instruction from the program counter (PC) address and store it in the IR. It also increments the PC by 1 to point to the next instruction. In the decode state, the control unit decodes the opcode data in the IR and determines the type and format of the instruction. It also sends signals to read the operands from the registers or memory as specified by the instruction. In the execute state, the control unit sends signals to the ALU to perform the required arithmetic or logical operation on the operands and produce a result. It also sets or clears some flags based on the outcome of the operation. The execute state can be broken down into specific instruction states. For example, a load instructions execution state can be broken down into 5 separate substates, where different signals are sent out sequentially in order to properly execute the instruction.

The control unit can also handle different types of instructions such as R-type, I-type, J-type, etc. Each type of instruction has a different format and requires different control signals. For example, an R-type instruction has three register operands (Ra, Rb, Rc) and an ALU operation code. An I-type instruction has two register operands (Ra, Rb) and an immediate value. A J-type instruction has a jump address. The control unit can decode these formats and send appropriate signals to execute them.

One of the instructions that the control unit can handle is Xor, which performs a bitwise exclusive OR operation on two operands. The Xor instruction was not part of the original CPU specs document, but it was added later. The Xor instruction was implemented by adding a new IR opcodes (11110 in the first 5 bits), a new XOR alu function, and new XOR execution states to the control unit.

```
//Control unit for CPU
//Finite state machine logic for control
`timescale 1ns/1ps
module ctrl_unit(
    //Test Bench inputs/outputs but goes through datapath
    input clk, reset, stop,
    output reg run, clear,
    //Datapath inputs/outputs
    input [31:0] IRdata,
    output reg read, write,
    output reg BAout, Rin, Rout,
    output reg Gra, Grb, Grc,
    output reg CONN_in,
```

```

output reg MARin, MDRin,
output reg HIin, LOin,
output reg Yin, Zin,
output reg PCin, IRin, incPC,
output reg InPortIn, OutPortIn,
output reg HIout, LOout, ZLowOut, ZHighOut,
output reg MDRout, Cout, InPortOut, PCout,
output reg [4:0] alu_opcode,
output reg jal_flag
);

wire [4:0] ir_op;

assign ir_op = IRdata[31:27];

//Control unit states
parameter reset_state = 8'b00000000,
//Fetch states
fetch0 = 8'b00000001, fetch1 = 8'b00000010, fetch2= 8'b00000011,
//Add states
add3 = 8'b00000100, add4= 8'b00000101, add5= 8'b00000110,
//Sub states
sub3 = 8'b00000111, sub4 = 8'b00001000, sub5 = 8'b00001001,
//Multiplication states
mul3 = 8'b00001010, mul4 = 8'b00001011, mul5 = 8'b00001100, mul6 =
8'b00001101,
//Division states
div3 = 8'b00001110, div4 = 8'b00001111, div5 = 8'b00010000, div6 = 8'b00010001,
//Or states
or3 = 8'b00010010, or4 = 8'b00010011, or5 = 8'b00010100,
//Xor states
xor3 = 8'b10010101, xor4 = 8'b10010110, xor5 = 8'b10011111,
//And states
and3 = 8'b00010101, and4 = 8'b00010110, and5 = 8'b00010111,
//Shift left states
shl3 = 8'b00011000, shl4 = 8'b00011001, shl5 = 8'b00011010,
//Shift right states
shr3 = 8'b00011011, shr4 = 8'b00011100, shr5 = 8'b00011101,
//Shift right arithmetic states
shra3 = 8'b10011011, shra4 = 8'b10011100, shra5 = 8'b10011101,
//Rotate left states
rol3 = 8'b00011110, rol4 = 8'b00011111, rol5 = 8'b00100000,
//Rotate right states
ror3 = 8'b00100001, ror4 = 8'b00100010, ror5 = 8'b00100011,
//Negate states
neg3 = 8'b00100100, neg4 = 8'b00100101, neg5 = 8'b00100110,

```

```

        //Not states
        not3 = 8'b00100111, not4 = 8'b00101000, not5 = 8'b00101001,
        //Load states
        ld3 = 8'b00101010, ld4 = 8'b00101011, ld5 = 8'b00101100, ld6 = 8'b00101101,
ld7 = 8'b00101110,
        //Load immediate states
        ldi3 = 8'b00101111, ldi4 = 8'b00110000, ldi5 = 8'b00110001,
        //Store States
        st3 = 8'b00110010, st4 = 8'b00110011, st5 = 8'b00110100, st6 = 8'b00110101,
st7 = 8'b00110110,
        //Add immediate states
        addi3 = 8'b00110111, addi4 = 8'b00111000, addi5 = 8'b00111001,
        //And immediate states
        andi3 = 8'b00111010, andi4 = 8'b00111011, andi5 = 8'b00111100,
        //Or immediate states
        ori3 = 8'b00111101, ori4 = 8'b00111110, ori5 = 8'b00111111,
        //Branch if States
        br3 = 8'b01000000, br4 = 8'b01000001, br5 = 8'b01000010, br6 = 8'b01000011,
        //Move reg to PC state
        jrr3 = 8'b01000100,
        //Move PC to reg state
        jal3 = 8'b01000101, jal4 = 8'b10000001,
        //Move HI to reg state
        mfhi3 = 8'b01000111,
        //Move LO to reg state
        mflo3 = 8'b01001000,
        //Move Inport to reg state
        in3 = 8'b01001001,
        //Move reg to Outport state
        out3 = 8'b01001010,
        //No operation state (go to fetch0)
        nop3 = 8'b01001011,
        //Halt state
        halt = 8'b01001100;

//ALU opcodes
parameter alu_nop = 5'b00000,
        alu_addop = 5'b00001,
        alu_subop = 5'b00010,
        alu_mulop = 5'b00011,
        alu_divop = 5'b00100,
        alu_shrop = 5'b00101,
        alu_shlop = 5'b00110,
        alu_shraop = 5'b00111,
        alu_rorop = 5'b01000,

```

```
alu_rolop = 5'b01001,  
alu_andop = 5'b01010,  
alu_orop = 5'b01011,  
alu_negop = 5'b01100,  
alu_xorop = 5'b01101,  
alu_norop = 5'b01110,  
alu_notop = 5'b01111;
```

```
//IR opcodes
```

```
parameter ir_add = 5'b00011,  
ir_sub = 5'b00100,  
ir_mul = 5'b01111,  
ir_div = 5'b10000,  
ir_shl = 5'b01001,  
ir_shr = 5'b00111,  
ir_shra = 5'b01000,  
ir_rol = 5'b01011,  
ir_ror = 5'b01010,  
ir_and = 5'b00101,  
ir_or = 5'b00110,  
ir_xor = 5'b11110, //Xor opcode is 11110  
ir_neg = 5'b10001,  
ir_not = 5'b10010,  
ir_ld = 5'b00000,  
ir_ldi = 5'b00001,  
ir_st = 5'b00010,  
ir_addi = 5'b01100,  
ir_andi = 5'b01101,  
ir_ori = 5'b01110,  
ir_br = 5'b10011,  
ir_jr = 5'b10100,  
ir_jal = 5'b10101,  
ir_mfhi = 5'b11000,  
ir_mflo = 5'b11001,  
ir_in = 5'b10110,  
ir_out = 5'b10111,  
ir_nop = 5'b11010,  
ir_halt = 5'b11011;
```

```
reg [7:0] present_state = halt;
```

```
always @(posedge clk, posedge reset, posedge stop) begin
```

```
    if (reset) begin //reset the processor
```

```
        #5 present_state = reset_state;
```

```
        #10 present_state = fetch0;
```

```
    end
```

```
    if (stop) begin
```

```
        present_state = halt;
```

```
    end
```

```
    case (present_state)
```

```
        fetch0 : #40 present_state = fetch1;
```

```
        fetch1 : #40 present_state = fetch2;
```

```
        fetch2 : begin
```

```
            #40
```

```
            case (ir_op)
```

```
                ir_add : present_state = add3;
```

```
                ir_sub : present_state = sub3;
```

```
                ir_mul : present_state = mul3;
```

```
                ir_div : present_state = div3;
```

```
                ir_shl : present_state = shl3;
```

```
                ir_shr : present_state = shr3;
```

```
                ir_shra : present_state = shra3;
```

```
                ir_rol : present_state = rol3;
```

```
                ir_ror : present_state = ror3;
```

```
                ir_and : present_state = and3;
```

```
                ir_or : present_state = or3;
```

```
                ir_xor : present_state = xor3;
```

```
                ir_neg : present_state = neg3;
```

```
                ir_not : present_state = not3;
```

```
                ir_ld : present_state = ld3;
```

```
                ir_ldi : present_state = ldi3;
```

```
                ir_st : present_state = st3;
```

```
                ir_addi : present_state = addi3;
```

```
                ir_andi : present_state = andi3;
```

```
                ir_ori : present_state = ori3;
```

```
                ir_br : present_state = br3;
```

```
                ir_jr : present_state = jr3;
```

```
                ir_jal : present_state = jal3;
```

```
                ir_mfhi : present_state = mfhi3;
```

```
                ir_mflo : present_state = mflo3;
```

```
                ir_in : present_state = in3;
```

```
                ir_out : present_state = out3;
```

```
                ir_nop : present_state = fetch0;
```



```

        ir_halt : present_state = halt;
    endcase
end
//Add instruction
add3    : #40 present_state = add4;
add4    : #40 present_state = add5;
add5    : #40 present_state = fetch0;

//Sub instruction
sub3    : #40 present_state = sub4;
sub4    : #40 present_state = sub5;
sub5    : #40 present_state = fetch0;

//Mul instruction
mul3    : #40 present_state = mul4;
mul4    : #40 present_state = mul5;
mul5    : #40 present_state = mul6;
mul6    : #40 present_state = fetch0;

//Div instruction
div3    : #40 present_state = div4;
div4    : #40 present_state = div5;
div5    : #40 present_state = div6;
div6    : #40 present_state = fetch0;

//Or instruction
or3     : #40 present_state = or4;
or4     : #40 present_state = or5;
or5     : #40 present_state = fetch0;

//Xor instruction
xor3    : #40 present_state = xor4;
xor4    : #40 present_state = xor5;
xor5    : #40 present_state = fetch0;

//And instruction
and3    : #40 present_state = and4;
and4    : #40 present_state = and5;
and5    : #40 present_state = fetch0;

//Shift left instructions
shl3    : #40 present_state = shl4;
shl4    : #40 present_state = shl5;
shl5    : #40 present_state = fetch0;

```

```
//Shift right instructions
shr3   : #40 present_state = shr4;
shr4   : #40 present_state = shr5;
shr5   : #40 present_state = fetch0;

//Shift right arithmetic instructions
shra3  : #40 present_state = shra4;
shra4  : #40 present_state = shra5;
shra5  : #40 present_state = fetch0;

//Rotate left instructions
rol3   : #40 present_state = rol4;
rol4   : #40 present_state = rol5;
rol5   : #40 present_state = fetch0;

//Rotate right instructions
ror3   : #40 present_state = ror4;
ror4   : #40 present_state = ror5;
ror5   : #40 present_state = fetch0;

//Negate instructions
neg3   : #40 present_state = neg4;
neg4   : #40 present_state = neg5;
neg5   : #40 present_state = fetch0;

//Not instructions
not3   : #40 present_state = not4;
not4   : #40 present_state = not5;
not5   : #40 present_state = fetch0;

//Load instructions
ld3    : #40 present_state = ld4;
ld4    : #40 present_state = ld5;
ld5    : #40 present_state = ld6;
ld6    : #40 present_state = ld7;
ld7    : #40 present_state = fetch0;

//Load immediate instructions
ldi3   : #40 present_state = ldi4;
ldi4   : #40 present_state = ldi5;
ldi5   : #40 present_state = fetch0;

//Store instructions
st3    : #40 present_state = st4;
st4    : #40 present_state = st5;
```

```

st5      : #40 present_state = st6;
st6      : #40 present_state = st7;
st7      : #40 present_state = fetch0;

//Add immediate instructions
addi3    : #40 present_state = addi4;
addi4    : #40 present_state = addi5;
addi5    : #40 present_state = fetch0;

//And immediate instructions
andi3    : #40 present_state = andi4;
andi4    : #40 present_state = andi5;
andi5    : #40 present_state = fetch0;

//Or immediate instructions
ori3     : #40 present_state = ori4;
ori4     : #40 present_state = ori5;
ori5     : #40 present_state = fetch0;

//Branch instructions
br3      : #40 present_state = br4;
br4      : #40 present_state = br5;
br5      : #40 present_state = br6;
br6      : #40 present_state = fetch0;

//Jump register instructions
jr3      : #40 present_state = fetch0;

//Jump and link instructions
jal3     : #40 present_state = jal4;
jal4     : #40 present_state = fetch0;

//Move from HI instructions
mfhi3    : #40 present_state = fetch0;

//Move from LO instructions
mflo3    : #40 present_state = fetch0;

//Input instructions
in3      : #40 present_state = fetch0;

//Output instructions
out3     : #40 present_state = fetch0;

//If restart, go to halt

```

```

        reset_state : begin
            #40 present_state = fetch0;
        end

        //halt state
        halt : begin
            present_state = halt;
        end
    endcase

end

always @(present_state) begin
    case (present_state)
        reset_state : begin
            run = 1; clear = 1;
            read = 0; write = 0;
            Gra = 0; Grb = 0; Grc = 0; Rin = 0;
            BAout = 0; Rin = 0; Rout = 0;
            CONN_in = 0;
            MARin = 0; MDRin = 0;
            HIin = 0; LOin = 0;
            Yin = 0; Zin = 0;
            PCin = 0; IRin = 0; incPC = 0;
            InPortIn = 0; OutPortIn = 0;
            jal_flag = 0;
            HIout = 0; LOout = 0; ZLowOut = 0; ZHighOut = 0;
            MDRout = 0; Cout = 0; InPortOut = 0; PCout = 0;
            #3 clear = 0; run = 0;
        end

        fetch0: begin
            #10 PCout = 1; MARin = 1; Zin = 1; incPC = 1;
            #15 PCout = 0; MARin = 0; Zin = 0; incPC = 0;
        end

        fetch1: begin
            #10 ZLowOut = 1; PCin = 1; read = 1; MDRin = 1;
            #15 ZLowOut = 0; PCin = 0; read = 0; MDRin = 0;
        end

        fetch2: begin
            #10 MDRout = 1; IRin = 1;
            #10 MDRout = 0; IRin = 0;
        end

        //Alu instruction states
    endcase
end

```

```

        add3, sub3, and3, or3, shl3, shr3, shra3, ror3, rol3, addi3, andi3, ori3, neg3,
not3, xor3: begin
    #10 Grb = 1; Rout = 1; Yin = 1;
    #15 Grb = 0; Rout = 0; Yin = 0;
end
mul3, div3: begin
    #10 Gra = 1; Rout = 1; Yin = 1;
    #15 Gra = 0; Rout = 0; Yin = 0;
end
add4 : begin
    #10 Zin = 1; Grc = 1; Rout = 1; alu_opcode = alu_addop;
    #15 Zin = 0; Grc = 0; Rout = 0; alu_opcode = alu_nop;
end
sub4 : begin
    #10 Zin = 1; Grc = 1; Rout = 1; alu_opcode = alu_subop;
    #15 Zin = 0; Grc = 0; Rout = 0; alu_opcode = alu_nop;
end
and4 : begin
    #10 Zin = 1; Grc = 1; Rout = 1; alu_opcode = alu_andop;
    #15 Zin = 0; Grc = 0; Rout = 0; alu_opcode = alu_nop;
end
or4 : begin
    #10 Zin = 1; Grc = 1; Rout = 1; alu_opcode = alu_orop;
    #15 Zin = 0; Grc = 0; Rout = 0; alu_opcode = alu_nop;
end
xor4 : begin
    #10 Zin = 1; Grc = 1; Rout = 1; alu_opcode = alu_xorop;
    #15 Zin = 0; Grc = 0; Rout = 0; alu_opcode = alu_nop;
end
shl4 : begin
    #10 Zin = 1; Grc = 1; Rout = 1; alu_opcode = alu_shlop;
    #15 Zin = 0; Grc = 0; Rout = 0; alu_opcode = alu_nop;
end
shr4 : begin
    #10 Zin = 1; Grc = 1; Rout = 1; alu_opcode = alu_shrop;
    #15 Zin = 0; Grc = 0; Rout = 0; alu_opcode = alu_nop;
end
shra4 : begin
    #10 Zin = 1; Grc = 1; Rout = 1; alu_opcode = alu_shraop;
    #15 Zin = 0; Grc = 0; Rout = 0; alu_opcode = alu_nop;
end
ror4 :begin
    #10 Zin = 1; Grc = 1; Rout = 1; alu_opcode = alu_rorop;
    #15 Zin = 0; Grc = 0; Rout = 0; alu_opcode = alu_nop;
end
end

```

```

rol4 : begin
    #10 Zin = 1; Grc = 1; Rout = 1; alu_opcode = alu_rolop;
    #15 Zin = 0; Grc = 0; Rout = 0; alu_opcode = alu_nop;
end
addi4 :begin
    #10 Zin = 1; Cout = 1; alu_opcode = alu_addop;
    #15 Zin = 0; Cout = 0; alu_opcode = alu_nop;
end
andi4 : begin
    #10 Zin = 1; Cout = 1; alu_opcode = alu_andop;
    #15 Zin = 0; Cout = 0; alu_opcode = alu_nop;
end
ori4 : begin
    #10 Zin = 1; Cout = 1; alu_opcode = alu_orop;
    #15 Zin = 0; Cout = 0; alu_opcode = alu_nop;
end
mul4 : begin
    #10 Zin = 1; Grb = 1; Rout = 1; alu_opcode = alu_mulop;
    #15 Zin = 0; Grb = 0; Rout = 0; alu_opcode = alu_nop;
end
div4 : begin
    #10 Zin = 1; Grb = 1; Rout = 1; alu_opcode = alu_divop;
    #15 Zin = 0; Grb = 0; Rout = 0; alu_opcode = alu_nop;
end
neg4 : begin
    #10 Zin = 1; alu_opcode = alu_negop;
    #15 Zin = 0; alu_opcode = alu_nop;
end
not4 : begin
    #10 Zin = 1; alu_opcode = alu_notop;
    #15 Zin = 0; alu_opcode = alu_nop;
end
add5, sub5, and5, or5, shl5, shr5, shra5, ror5, rol5, andi5, addi5, ori5, not5,
neg5, xor5: begin
    #10 ZLowOut = 1; Gra = 1; Rin = 1;
    #15 ZLowOut = 0; Gra = 0; Rin = 0;
end
mul5, div5 : begin
    #10 ZLowOut = 1; LOin = 1; Rin = 1;
    #15 ZLowOut = 0; LOin = 0; Rin = 0;
end
mul6, div6 : begin
    #10 ZHighOut = 1; HIin = 1; Rin = 1;
    #15 ZHighOut = 0; HIin = 0; Rin = 0;
end

```

```

//Load instruction states
ld3, ldi3: begin
    #10 Grb = 1; BAout = 1; Yin = 1;
    #10 Grb = 0; BAout = 0; Yin = 0;
end
ld4, ldi4 : begin
    #10 Zin = 1; Cout = 1; alu_opcode = alu_addop;
    #15 Zin = 0; Cout = 0; alu_opcode = alu_nop;
end
ld5 : begin
    #10 ZLowOut = 1; MARin = 1;
    #15 ZLowOut = 0; MARin = 0;
end
ldi5 : begin
    #10 ZLowOut = 1; Rin = 1; Gra = 1;
    #15 ZLowOut = 0; Rin = 0; Gra = 0;
end
ld6 : begin
    #10 read = 1; MDRin = 1;
    #15 read = 0; MDRin = 0;
end
ld7 : begin
    #10 MDRout = 1; Rin = 1; Gra = 1;
    #15 MDRout = 0; Rin = 0; Gra = 0;
end

//Store instruction states
st3 : begin
    #10 Grb = 1; BAout = 1; Yin = 1;
    #10 Grb = 0; BAout = 0; Yin = 0;
end
st4: begin
    #10 Zin = 1; Cout = 1; alu_opcode = alu_addop;
    #15 Zin = 0; Cout = 0; alu_opcode = alu_nop;
end
st5 : begin
    #10 ZLowOut = 1; MARin = 1;
    #15 ZLowOut = 0; MARin = 0;
end
st6 : begin
    #10 write = 1; MDRin = 1; Rout = 1; Gra = 1;
    #15 write = 0; MDRin = 0; Rout = 0; Gra = 0;
end

```

```

//Branch instruction states
br3: begin
    #10 Gra = 1; Rout = 1;
    #15 Gra = 0; Rout = 0;
end
br4: begin
    #10 PCout = 1; Yin = 1;
    #15 PCout = 0; Yin = 0;
end
br5: begin
    #10 Cout = 1; Zin = 1; CONN_in = 1; alu_opcode = alu_nop;
    #15 Cout = 0; Zin = 0; CONN_in = 0;
end
br6: begin
    #10 ZLowOut = 1; PCin = 1;
    #15 ZLowOut = 0; PCin = 0;
end

//Jump register and Jump and Link Register instructions
jr3 : begin
    #10 Gra = 1; Rout = 1; PCin = 1;
    #10 Gra = 0; Rout = 0; PCin = 0;
end
jal3 : begin
    #10 PCout = 1; jal_flag = 1;
    #10 PCout = 0; jal_flag = 0;
end
jal4: begin
    #10 PCin = 1; Gra = 1; Rout = 1;
    #10 PCin = 0; Gra = 0; Rout = 0;
end

//Input Output instruction states
in3: begin
    #10 InPortIn = 1; Rin = 1; Gra = 1;
    #15 InPortIn = 0; Rin = 0; Gra = 0;
end
out3: begin
    #10 OutPortIn = 1; Rout = 1; Gra = 1;
    #15 OutPortIn = 0; Rout = 0; Gra = 0;
end

//Mfhi and Mflo instruction states
mfhi3: begin
    #10 HIout = 1; Rin = 1; Gra = 1;

```



```
        #15 HIout = 0; Rin = 0; Gra = 0;
    end
    mflo3: begin
        #10 LOout = 1; Rin = 1; Gra = 1;
        #15 LOout = 0; Rin = 0; Gra = 0;
    end

    //No operation instruction states
    nop3: begin
        #10 alu_opcode = alu_nop;
    end

    //If halted, show that not running
    halt: begin
        run = 0;
        clear = 0;
    end
endcase
end

endmodule
```

The Datapath

The Datapath module is the part of the processor that connects all components and is the highest-level entity. It consists of registers, ALU, bus, and multiplexers.

To integrate the control unit into the datapath module, we made some changes to the inputs and outputs of the datapath. The datapath now only takes inputs for clock, clear, and stop. These are signals that control the timing, resetting, and halting of the processor. It also takes in the InPortData, which is the data from the input port. The datapath outputs run, and OutPortData. The run signal indicates whether the processor is executing an instruction or not. The OutPortData is the data to be sent to the output port.

The control unit uses the Jal_flag and or's it with R15in so that when doing a jump and link instruction the R15 value stores the PC value as a return register. The Jal_flag is a signal that indicates whether the current instruction is a jump and link instruction or not. The R15 in is the input to register 15 from the multiplexer. The PC value is the value of the program counter register, which holds the address of the next instruction to be executed. By or'ing the Jal_flag with R15 in, we ensure that register 15 will store the PC value only when executing a jump and link instruction. This way, register 15 can be used as a return address for subroutine calls.

```
module datapath (  
    //Test Bench inputs/outputs but goes through datapath to control unit  
    output run,  
    input wire clk, reset, stop,  
    //Inport data from external device  
    input [31:0] InPortData  
);  
  
wire clr;  
  
wire R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out,  
R12out, R13out, R14out, R15out;  
wire R0in, R1in, R2in, R3in, R4in, R5in, R6in, R7in, R8in, R9in, R10in, R11in, R12in, R13in,  
R14in, R15in;  
wire branch_flag;  
//control unit wires  
wire PCout, read, write, BAout, Rin, Rout, Gra, Grb, Grc, CONN_in, MARin, MDRin, HIin, LOin,  
Yin, jal_flag, R15jal,  
    Zin, PCin, IRin, incPC, InPortIn, OutPortIn, HIout, LOout, ZLowOut, ZHighOut, MDRout,  
Cout, InPortOut;  
wire [4:0] opcode;  
  
wire [31:0] BusMuxIn_R0,  
    BusMuxIn_R1,  
    BusMuxIn_R2,  
    BusMuxIn_R3,  
    BusMuxIn_R4,
```

```

        BusMuxIn_R5,
        BusMuxIn_R6,
        BusMuxIn_R7,
        BusMuxIn_R8,
        BusMuxIn_R9,
        BusMuxIn_R10,
        BusMuxIn_R11,
        BusMuxIn_R12,
        BusMuxIn_R13,
        BusMuxIn_R14,
        BusMuxIn_R15;

wire [31:0] IRdata,
        BusMuxIn_HI,
        BusMuxIn_LO,
        BusMuxIn_Zhigh,
        BusMuxIn_Zlow,
        BusMuxIn_PC,
        BusMuxIn_MDR,
        BusMuxIn_InPort,
        RamDataOut,
        Yout,
        d_pc,
        MARout,
        BusMuxOut,
        C_sign_extended,
        OutPortOut;

wire [63:0] CRegOut;

//Control unit initialization
ctrl_unit cu (
    //Test Bench inputs/outputs but goes through datapath
    .run(run),
    .clear(clr),
    .clk(clk),
    .reset(reset),
    .stop(stop),
    //Datapath inputs/outputs
    .IRdata(IRdata),
    .read(read),
    .write(write),
    .BAout(BAout),
    .Rin(Rin),

```

```

        .Rout(Rout),
        .Gra(Gra),
        .Grb(Grb),
        .Grc(Grc),
        .CONN_in(CONN_in),
        .MARin(MARin),
        .MDRin(MDRin),
        .HIin(HIin),
        .LOin(LOin),
        .Yin(Yin),
        .Zin(Zin),
        .PCin(PCin),
        .IRin(IRin),
        .incPC(incPC),
        .InPortIn(InPortIn),
        .OutPortIn(OutPortIn),
        .HIout(HIout),
        .LOout(LOout),
        .ZLowOut(ZLowOut),
        .ZHighOut(ZHighOut),
        .MDRout(MDRout),
        .Cout(Cout),
        .InPortOut(InPortOut),
        .PCout(PCout),
        .alu_opcode(opcode),
        .jal_flag(jal_flag)
    );

assign R15jal = (R15in | jal_flag);

regR0 R0 (BAout, clr, clk, R0in, BusMuxOut, BusMuxIn_R0); //input signal is always 0 for R0
(special reg)
reg32bit R2 (clr, clk, R2in, BusMuxOut, BusMuxIn_R2);
reg32bit R3 (clr, clk, R3in, BusMuxOut, BusMuxIn_R3);
reg32bit R1 (clr, clk, R1in, BusMuxOut, BusMuxIn_R1);
reg32bit R4 (clr, clk, R4in, BusMuxOut, BusMuxIn_R4);
reg32bit R5 (clr, clk, R5in, BusMuxOut, BusMuxIn_R5);
reg32bit R6 (clr, clk, R6in, BusMuxOut, BusMuxIn_R6);
reg32bit R7 (clr, clk, R7in, BusMuxOut, BusMuxIn_R7);
reg32bit R8 (clr, clk, R8in, BusMuxOut, BusMuxIn_R8);
reg32bit R9 (clr, clk, R9in, BusMuxOut, BusMuxIn_R9);
reg32bit R10 (clr, clk, R10in, BusMuxOut, BusMuxIn_R10);
reg32bit R11 (clr, clk, R11in, BusMuxOut, BusMuxIn_R11);
reg32bit R12 (clr, clk, R12in, BusMuxOut, BusMuxIn_R12);
reg32bit R13 (clr, clk, R13in, BusMuxOut, BusMuxIn_R13);

```

```

reg32bit R14 (clr, clk, R14in, BusMuxOut, BusMuxIn_R14);
reg32bit R15 (clr, clk, R15jal, BusMuxOut, BusMuxIn_R15);

reg32bit HI (clr, clk, HIin, BusMuxOut, BusMuxIn_HI);
reg32bit LO (clr, clk, LOin, BusMuxOut, BusMuxIn_LO);
reg32bit ZHigh (clr, clk, Zin, CRegOut[63:32], BusMuxIn_Zhigh);
reg32bit ZLow (clr, clk, Zin, CRegOut[31:0], BusMuxIn_Zlow);

//PC reg initialization, using specific incPC input to increment PC by 1 each time set to high
regPC PC (clr, clk, PCin, BusMuxOut, BusMuxIn_PC);

//Input and output ports added to datapath (p2)
reg32bit InPort (clr, clk, InPortIn, InPortData, BusMuxIn_InPort);
reg32bit OutPort (clr, clk, OutPortIn, BusMuxOut, OutPortOut);

//MDR reg initialization

MD_reg32 MDR (.clr(clr), .clk(clk), .read(read), .MDRin(MDRin), .BusMuxOut(BusMuxOut),
.Mdatain(RamDataOut), .Q(BusMuxIn_MDR)); //special MDR reg
reg32bit MAR (clr, clk, MARin, BusMuxOut, MARout);

// Goes into ALU A input
reg32bit Y (clr, clk, Yin, BusMuxOut, Yout);

//Instruction register. IRdata doesn't go on the bus, but leads to CON
reg32bit IR (clr, clk, IRin, BusMuxOut, IRdata);

//Memory initialization
//RamDataOut used as MDR input since, using BusMuxIn_MDR would have two registers writing to
the same input.
ram myRam (.clk(clk), .read(read), .write(write), .MARout(MARout[8:0]), .D(BusMuxIn_MDR),
.Q(RamDataOut));

//Control Branch logic
CONN_FF myConn_ff (
    .IRdata(IRdata),
    .BusMuxOut(BusMuxOut),
    .CONN_in(CONN_in),
    .CONN_out(branch_flag)
);

//Select and Encode logic for selecting register functions based on opcode
select_and_encode mySAE (

```

```
.irOut(IRdata),
.Gra(Gra),
.Grb(Grb),
.Grc(Grc),
.Rin(Rin),
.Rout(Rout),
.BAout(BAout),
.R0in(R0in),
.R1in(R1in),
.R2in(R2in),
.R3in(R3in),
.R4in(R4in),
.R5in(R5in),
.R6in(R6in),
.R7in(R7in),
.R8in(R8in),
.R9in(R9in),
.R10in(R10in),
.R11in(R11in),
.R12in(R12in),
.R13in(R13in),
.R14in(R14in),
.R15in(R15in),
.R0out(R0out),
.R1out(R1out),
.R2out(R2out),
.R3out(R3out),
.R4out(R4out),
.R5out(R5out),
.R6out(R6out),
.R7out(R7out),
.R8out(R8out),
.R9out(R9out),
.R10out(R10out),
.R11out(R11out),
.R12out(R12out),
.R13out(R13out),
.R14out(R14out),
.R15out(R15out),
.C_sign_extended(C_sign_extended)
);

//bus
bus myBus (
    //encoder
```

```
.R0out(R0out),
.R1out(R1out),
.R2out(R2out),
.R3out(R3out),
.R4out(R4out),
.R5out(R5out),
.R6out(R6out),
.R7out(R7out),
.R8out(R8out),
.R9out(R9out),
.R10out(R10out),
.R11out(R11out),
.R12out(R12out),
.R13out(R13out),
.R14out(R14out),
.R15out(R15out),
.HIout(HIout),
.L0out(L0out),
.ZHighOut(ZHighOut),
.ZLowOut(ZLowOut),
.PCout(PCout),
.MDRout(MDRout),
.InPortOut(InPortOut),
.Cout(Cout),
//multiplexer
.BusMuxIn_R0(BusMuxIn_R0),
.BusMuxIn_R1(BusMuxIn_R1),
.BusMuxIn_R2(BusMuxIn_R2),
.BusMuxIn_R3(BusMuxIn_R3),
.BusMuxIn_R4(BusMuxIn_R4),
.BusMuxIn_R5(BusMuxIn_R5),
.BusMuxIn_R6(BusMuxIn_R6),
.BusMuxIn_R7(BusMuxIn_R7),
.BusMuxIn_R8(BusMuxIn_R8),
.BusMuxIn_R9(BusMuxIn_R9),
.BusMuxIn_R10(BusMuxIn_R10),
.BusMuxIn_R11(BusMuxIn_R11),
.BusMuxIn_R12(BusMuxIn_R12),
.BusMuxIn_R13(BusMuxIn_R13),
.BusMuxIn_R14(BusMuxIn_R14),
.BusMuxIn_R15(BusMuxIn_R15),
.BusMuxIn_HI(BusMuxIn_HI),
.BusMuxIn_L0(BusMuxIn_L0),
.BusMuxIn_Zhigh(BusMuxIn_Zhigh),
.BusMuxIn_Zlow(BusMuxIn_Zlow),
```

```

        .BusMuxIn_PC(BusMuxIn_PC),
        .BusMuxIn_MDR(BusMuxIn_MDR),
        .BusMuxIn_InPort(BusMuxIn_InPort),
        .C_sign_extended(C_sign_extended),
        .BusMuxOut(BusMuxOut)
    );

//alu
alu_test myAlu(
    .clk(clk),
    .clr(clr),
    .incPC(incPC),
    .CONN_out(branch_flag),
    .B(BusMuxOut),
    .A(Yout),
    .opcode(opcode),
    .C(CRegOut)
);
endmodule

```

Xor Module (Bonus)

A new module for Xor'ing two 32 bit values was wired into the ALU and given its own opcode. The module code is as follows:

```

module xor32 (a,b,c);
    input wire [31:0]a,b;
    output reg [31:0]c;
    integer i;

    always @(*)begin
        for (i = 0; i < 32; i = i + 1) begin
            c[i] = ((a[i])^(b[i]));
        end
    end
endmodule

```


Updated Ram

The ram was updated to read in the ram.hex file. The `ifdef and `endif code was the new added lines that read the file in when initializing RAM.

```
//512 x 32 RAM
module ram(
    input clk, read, write,
    input [8:0] MARout,      //address
    input [31:0] D,
    output [31:0] Q
);
    reg [31:0] mem [511:0];

    `ifdef MODEL_TECH
    initial $readmemh("../ram.hex", mem);
    `else
    initial $readmemh("ram.hex", mem);
    `endif

    assign Q = (write || !read) ? 32'bZZZZZZZZ : mem[MARout];

    always @(posedge clk) begin
        if(write) mem[MARout] = D;
    end
endmodule
```

Testbench

This is a test bench for a Verilog module called `tb_minisrc`. It simulates the behavior of the datapath module by providing inputs and observing outputs. The test bench sets up an initial state for the simulation by initializing the inputs clock, reset, stop, and InPortData. The clock signal is toggled every 2 time units to drive the simulation. The reset signal is asserted for 2 time units at the beginning of the simulation to reset the datapath module.

The code for the testbench is as follows:

```
// Running the simulation outlined in CPU_Phase3

`timescale 1ns/1ps

module tb_minisrc;
    //Inputs
    reg clock;
    reg [31:0] InPortData;
    //Outputs
    reg reset, stop;
    //wire clear;
    wire run;

    datapath dp (
        .run(run),
        .clk(clock),
        .reset(reset),
        .stop(stop),
        // .clr(clear),
        .InPortData(InPortData)
    );

    initial begin
        #2 clock = 0; reset = 1; stop = 0; InPortData = 0;
        #2 reset = 0;
        #2 stop = 0;

    end
    always
        #2 clock = ~clock;
endmodule
```

The instruction that were pre-loaded into the memory are as follows:

```
0: ldi R1, 2
1: ldi R0, 0(R1)
2: ld R2, 104
3: ldi R2, -4(R2)
4: ld R1, 1(R2)
5: ldi R3, 105
6: brmi R3, 4
7: ldi R3, 2(R3)
8: ld R7, -3(R3)
9: nop
10: brpl R7, 2
11: ldi R2, 5
12: ldi R3, 2(R1)
13: add R3, R2, R3
14: addi R7, R7, 2
15: neg R7, R7
16: not R7, R7
17: andi R7, R7, 15
18: ror R1, R1, R0
19: ori R7, R1, 28
20: shra R7, R7, R0
21: shr R2, R3, R0
22: st 82, R2
23: rol R2, R2, R0
24: or R2, R3, R0
25: and R1, R2, R1
26: st 96(R1), R3
27: sub R3, R2, R3
28: shl R1, R2, R0
29: ldi R4, 6
30: ldi R5, 50
31: mul R5, R4
32: mfhi R7
33: mflo R6
34: div R5, R4
35: ldi R8, -1(R4)
36: ldi R9, -19(R5)
37: ldi R10, 0(R6)
38: ldi R11, 0(R7)
39: jal R10
40: xor R1, R2, R3
41: halt
82: 00000026 (immediate value in hex)
```

104: 00000055 (immediate value in hex)

240: 0000FFFF (immediate value in hex)

300: add R13, R8, R10

301: sub R12, R9, R11

302: sub R13, R13, R12

303: jr R15

Note that the value on the left hand side is the decimal representation of the address in memory where the value or instruction was loaded into. Some of the values were immediate values that were to be loaded into register. These were located at 82, 104, and 240 in memory.

The testbench had the following output in the wave form and memory viewer.

 


Figure 1: Entire waveform of all instructions.



 


Figure 4: Instructions 13 -18 (note 12 is skipped due to branch)

 


Figure 5: Instructions 19 to 23

 


Figure 6: Instruction 24 to 28

 


Figure 7: Instruction 29 to 34

 


Figure 8: Instruction 35 to 40

 


Figure 9: Instruction 300 to 304 then back to 40 - 42 (halt)

 


Figure 10: Contents of Memory after the program ran.